

CONTENTS

UNIT I

SEMICONDUCTOR DEVICES

1.1 - 1.109

1.1. Introduction	1.1
1.2. Energy-Band Theory.....	1.1
1.2.1. Energy Band Diagram.....	1.3
1.3. Semiconductors.....	1.6
1.4. PN Diode.....	1.10
1.4.1. Operation of a PN Junction Diode.....	1.12
1.4.2. Forward Biased PN Junction	1.13
1.4.3. Reverse Biased p – n Junction.....	1.14
1.4.4. PN Diode Symbol	1.16
1.4.5. V-I Characteristics of PN Diode.....	1.16
1.4.6. Static and Dynamic Resistance of a Diode	1.18
1.4.7. V- I Equation of a Diode.....	1.20
Solved Problems	1.22
1.4.8. Breakdown in Diodes.....	1.25
1.5. Energy Band Structure of Open Circuited PN Junction.....	1.29
1.6. Current Components in $p - n$ diode.....	1.32
1.7. Resistance of PN Diode	1.33
1.8. Temperature Dependence of PN diode.....	1.34
1.9. Transition or Space Charge or Depletion Capacitance	1.35
1.9.1. Linearly Graded Junction.....	1.39

1.10. Diffusion Capacitance.....	1.41
1.11. PN diode as Rectifier.....	1.43
1.11.1. Half-Wave Rectifier.....	1.44
1.11.2. Full –Wave Rectifier.....	1.49
1.11.3. Full Wave Bridge Rectifier.....	1.52
1.12. Zener Diode.....	1.53
1.12.1. Zener Diode as Voltage Regulator.....	1.57
Solved Problems	1.58
1.13. BJT.....	1.67
1.13.1. Introduction.....	1.67
1.13.2. Construction.....	1.67
1.13.3. Operation.....	1.68
1.13.4. Types of Configuration.....	1.72
1.13.5. CB Configuration.....	1.72
1.13.6. CE Configuration.....	1.76
1.13.7. CC Configuration.....	1.79
1.14. Field Effect Transistor.....	1.81
1.14.1. JFET.....	1.81
1.14.2. Construction of N-Channel JFET	1.81
1.14.3. Operation of N-Channel JFET	1.82
1.14.4. Characteristics Parameters of the JFET	1.86
1.15. Metal Oxide Semiconductor Field Effect Transistor (MOSFET)	1.88
1.15.1. Enhancement MOSFET	1.88
1.15.2. Depletion MOSFET.....	1.90
1.16. Unijunction Transistor (UJT).....	1.92

1.16.1. UJT Construction and Operation	1.92
1.16.2. UJT Characteristics.....	1.94
Two Marks Question and Answers.....	1.95
Review Questions.....	1.107

UNIT II

AMPLIFIERS	2.1 - 2.61
2.1. Introduction	2.1
2.2. Types of Amplifiers	2.1
2.2.1. Small Signal Amplifiers.....	2.1
2.3. Load Line and Operating Point	2.3
2.3.1 Biasing	2.3
2.4. Biasing method for BJT.....	2.7
2.4.1. Transistor Biasing	2.7
2.5. Biasing the FET	2.11
2.5.1. Biasing the MOSFET.....	2.14
2.6. BJT Small SIGNAL MODEL.....	2.15
2.6.1. Transistor as a two port device	2.15
2.6.2. Small Signal Analysis	2.17
2.6.3. Analysis of CE Amplifier	2.17
2.6.4. CE Amplifier with Emitter Resistor and Bypass Capacitance.....	2.20
2.6.5. Common Base (CB) Amplifier Analysis	2.24
2.6.6. Common Collector Amplifier	2.27
2.6.7. Comparison of CE, CB and CC Amplifiers.....	2.31
2.7. MOSFET Small Signal Model.....	2.32

2.7.1. Steps Involved in Small-Signal Analysis of MOSFET	2.33
2.7.2. MOSFET Common Source Small-Signal Amplifier Analysis	2.33
2.7.3. MOSFET Common Drain (Source Follower) Amplifier	2.36
2.8. Gain and Frequency Response of High Frequency analysis	2.39
2.8.1. Gain and Frequency Response of BJT Amplifier	2.39
2.8.2. Gain and Frequency Response of FET Amplifier.....	2.42
2.9. Frequency Response of Multistage Amplifiers.....	2.44
Solved Problems	2.46
Two Marks Question and Answers.....	2.57
Review Questions.....	2.60

UNIT III

MULTISTAGE AMPLIFIERS AND DIFFERENTIAL AMPLIFIER	3.1 - 3.63
---	-------------------

3.1. Introduction	3.1
3.2. BIMOS Amplifier	3.2
3.2.1. FET Cascade Amplifier	3.4
3.3. Differential Amplifier	3.5
3.3.1. Basic Differential Amplifier	3.8
3.3.2. Dual Input, Unbalanced Output Differential Amplifier.....	3.22
3.3.3. Single Input, Balanced Output Differential Amplifier	3.24
3.3.4. Single Input Unbalanced Output Differential Amplifier	3.25
3.4. FET Differential Amplifier.....	3.27
3.4.1. MOSFET Differential Pair.....	3.30
3.5. Tuned Amplifiers.....	3.31
3.5.1. Parallel Resonant Circuit	3.32

3.5.2. Small Signal Tuned Amplifiers	3.36
3.5.3. Single Tuned Amplifiers.....	3.37
3.5.4. Double-Tuned Voltage Amplifier.....	3.40
3.5.5. Stagger-Tuned Amplifier.....	3.41
Solved Problems	3.42
3.6. Neutralization	3.44
3.6.1. Neutralization Methods.....	3.45
3.6.2. Hazeltine Neutralization	3.45
3.6.3. Neutrodyne Neutralization.....	3.46
3.6.4. Rice Neutralization	3.47
3.6.5. Neutralization Using Coil	3.47
Solved Problems	3.48
Two Marks Question and Answers.....	3.58
Review Questions.....	3.62

UNIT IV

FEEDBACK AMPLIFIERS AND OSCILLATORS

4.1 - 4.42

4.1. Introduction	4.1
4.2. Basic Concept of Feedback.....	4.1
4.3. Effects of Negative Feedback	4.4
4.4. Types of Negative Feedback Connections.....	4.5
4.4.1. Voltage Series Feedback.....	4.6
4.4.2. Voltage Shunt Feedback	4.9
4.4.3. Current-Series Feedback.....	4.11
4.4.4. Current-Shunt Feedback	4.14

4.5. Introduction	4.16
4.6. Conditions for Oscillation (Barkhausen Criterion)	4.17
4.7. Hartley Oscillator.....	4.18
4.8. Colpits Oscillator.....	4.21
4.9. RC Oscillators.....	4.22
4.9.1. RC Phase Shift Oscillator	4.23
4.9.2. Wien Bridge Oscillator	4.25
4.10. Crystal Oscillators.....	4.27
Solved Problems	4.30
Two Mark Question and Answers	4.37
Review Questions.....	4.42

UNIT V

POWER AMPLIFIERS AND DC/DC CONVERTERS	5.1 - 5.65
--	-------------------

5.1. Introduction	5.1
5.1.1. Comparison of Small Signal and Large Signal Amplifiers	5.2
5.1.2. Classification of Power Amplifiers.....	5.4
5.2. Class A Power Amplifier	5.6
5.3. Transformer Coupled Class A Power Amplifiers	5.9
5.4. Class-B Power Amplifier	5.11
5.4.1. Class B Push Pull Power Amplifier	5.12
5.4.2. AC Output Power.....	5.15
5.4.3. Class B Complementary Symmetry Amplifiers	5.16
5.4.4. Comparison of Push Pull and Complementary Symmetry Amplifier ..	5.17
5.5. Class AB Amplifiers.....	5.18

5.6. Class C Power Amplifier	5.19
5.7. Distortion in Amplifiers	5.22
5.8. Comparison of Power Amplifiers	5.24
5.9. Power MOSFET	5.24
5.9.1. Construction.....	5.25
5.9.2. Operation.....	5.26
5.9.3. Characteristics.....	5.26
5.10. Temperature Effects	5.27
5.10.1. Comparison of Power MOSFET with Power BJT.....	5.28
5.11. Class AB Power Amplifier using MOSFET.....	5.28
5.11.1. Bias Circuit	5.29
5.11.2. Driver Circuit	5.30
5.12. DC to DC Converters	5.30
5.12.1. Applications	5.30
5.12.2. Operation of DC-DC Converter.....	5.31
5.12.3. Switching - Mode Regulator.....	5.32
5.13. Buck Regulator.....	5.32
5.14. Boost Regulator	5.38
5.15. Buck - Boost Converter.....	5.43
Solved Problems	5.48
Two Marks Question with Answers	5.60
Review Questions.....	5.65
Model Question Papers.....	MQ.1 - MQ.8